

## NILASAILA INSTITUTE OF SCIENCE & TECHNOLOGY SERGARH-756060, BALASORE (ODISHA) (Approved by AICTE& affiliated to SCTE&VT, Odisha)



## **LESSON PLAN**

SUBJECT: Th-2 (CIRCUIT & NETWORK THEORY )

## **CHAPTER WISE DISTRIBUTION OF PERIODS**

SI.No.	Name of the chapter as per the Syllabus	No. of Periods as per the Syllabus	No. of periods actually needed
1	Magnetic Circuits	7	7
2	Coupled Circuits	5	7
3	Circuit Elements And Analysis	6	10
4	Network Theorems	8	11
5	Ac Circuit And Resonance	8	10
6	Poly-phase Circuit	6	6
7	Transients	6	6
8	Two-Port Network	8	11
9	Filters	6	7
	Total Period:	60	75

Discipline: ELECTRICAL ENGINEERING	Semester: 3rd	Name of the Teaching Faculty: Er. Soumyajit Rout
Week	Class Day	Theory / Practical Topics
	1 <sup>st</sup>	MAGNETIC CIRCUITS 1 . 1 Introduction
	2 <sup>nd</sup>	1.2 Magnetizing force, Intensity, MMF, flux and their relations
1 <sup>st</sup>	3 <sup>rd</sup>	1 . 3 Permeability, reluctance and permeance
	4 <sup>th</sup>	1 . 4 Analogy between electric and Magnetic Circuits 1 . 5 B-H Curve
	5 <sup>th</sup>	1 . 6 Series & parallel magnetic circuit. 1 . 7 Hysteresis loop
	1 <sup>st</sup>	TUTORIAL CLASS
	2 <sup>nd</sup>	COUPLED CIRCUITS: 2 . 1 Self Inductance and Mutual Inductance
2 <sup>nd</sup>	3 <sup>rd</sup>	2 . 2 Conductively coupled circuit and mutual impedance
	4 <sup>th</sup>	2 . 3 Dot convention
	5 <sup>th</sup>	2 . 4 Coefficient of coupling
	1 <sup>st</sup>	2 . 5 Series and parallel connection of coupled inductors.
	2 <sup>nd</sup>	2 . 6 Solve numerical problems
3 <sup>rd</sup>	3 <sup>rd</sup>	TUTORIAL CLASS
	4 <sup>th</sup>	CIRCUIT ELEMENTS AND ANALYSIS: 3 . 1 Active, Passive, Unilateral & bilateral, Linear & Non linear elements

I		2 2 Mach Analysis Mach Equations by inspection
	5 <sup>th</sup>	3 . 2 Mesh Analysis, Mesh Equations by inspection
	1 <sup>st</sup>	3 . 3 Super mesh Analysis
	2 <sup>nd</sup>	3 . 4 Nodal Analysis, Nodal Equations by inspection
<b>4</b> <sup>th</sup>	3 <sup>rd</sup>	3 . 4 Nodal Analysis, Nodal Equations by inspection
	4 <sup>th</sup>	3 . 5 Super node Analysis
	5 <sup>th</sup>	3 . 6 Source Transformation Technique
	1 <sup>st</sup>	3 . 7 Solve numerical problems (With Independent Sources Only)
	2 <sup>nd</sup>	3 . 7 Solve numerical problems (With Independent Sources Only)
5 <sup>th</sup>	3 <sup>rd</sup>	TUTORIAL CLASS
	4 <sup>th</sup>	NETWORK THEOREMS: 4.1 Star to delta and delta to star transformation
	5 <sup>th</sup>	4.2 Super position Theorem
	1 <sup>st</sup>	4.2 Super position Theorem
	2 <sup>nd</sup>	4.3 Thevenin's Theorem
6 <sup>th</sup>	3 <sup>rd</sup>	4.3 Thevenin's Theorem
	4 <sup>th</sup>	4.4 Norton's Theorem

		4.5 Maximum power Transfer Theorem.
	5 <sup>th</sup>	
	1 <sup>st</sup>	4.5 Maximum power Transfer Theorem.
	2 <sup>nd</sup>	4.6 Solve numerical problems (With Independent Sources Only)
<b>7</b> <sup>th</sup>	3 <sup>rd</sup>	4.6 Solve numerical problems (With Independent Sources Only)
	4 <sup>th</sup>	TUTORIAL CLASS
	5 <sup>th</sup>	AC CIRCUIT AND RESONANCE: 5.1 A.C. through R-L, R-C & R-L-C Circuit
	1 <sup>st</sup>	5.2 Solution of problems of A.C. through R-L, R-C & R-L-C series Circuit by complex algebra method.
	2 <sup>nd</sup>	5.2 Solution of problems of A.C. through R-L, R-C & R-L-C series Circuit by complex algebra method.
8 <sup>th</sup>	3 <sup>rd</sup>	5.3 Solution of problems of A.C. through R-L, R-C & R-L-C parallel & Composite Circuits
	4 <sup>th</sup>	5.4 Power factor & power triangle.
	5 <sup>th</sup>	5.5 Deduce expression for active, reactive, apparent power.
	1 <sup>st</sup>	5.6 Derive the resonant frequency of series resonance and parallel resonance circuit
	2 <sup>nd</sup>	5.7 Define Bandwidth, Selectivity & Q-factor in series circuit.
9 <sup>th</sup>	3 <sup>rd</sup>	5.8 Solve numerical problems
	4 <sup>th</sup>	TUTORIAL CLASS

ı		
	5 <sup>th</sup>	POLYPHASE CIRCUIT 6.1 Concept of poly-phase system and phase sequence
	1 <sup>st</sup>	6.2 Relation between phase and line quantities in star & delta connectio
	2 <sup>nd</sup>	6.3 Power equation in 3-phase balanced circuit.
<b>10</b> <sup>th</sup>	3 <sup>rd</sup>	6.4 Solve numerical problems
	4 <sup>th</sup>	6.5 Measurement of 3-phase power by two wattmeter method.
	5 <sup>th</sup>	6.6 Solve numerical problems.
	1 <sup>st</sup>	TUTORIAL CLASS
	2 <sup>nd</sup>	TRANSIENTS: 7.1 Steady state & transient state response.
11 <sup>th</sup>	3 <sup>rd</sup>	7.2 Response to R-L, R-C & RLC circuit under DC condition.
	4 <sup>th</sup>	7.2 Response to R-L, R-C & RLC circuit under DC condition.
	5 <sup>th</sup>	7.3 Solve numerical problems
	1 <sup>st</sup>	7.3 Solve numerical problems
	2 <sup>nd</sup>	TUTORIAL CLASS
12 <sup>th</sup>	3 <sup>rd</sup>	TWO-PORT NETWORK: 8.1 Open circuit impedance (z) parameters
	4 <sup>th</sup>	8.2 Short circuit admittance (y) parameters

		8.3 Transmission (ABCD) parameters
	5 <sup>th</sup>	
		9.4 Underid (b) parameters
		8.4 Hybrid (h) parameters.
		8.5 Inter relationships of different parameters.
		8.5 Inter relationships of different parameters.
<b>13</b> <sup>th</sup>		
		8.6 T and π representation
		8.6 T and $\pi$ representation
		8.7 Solve numerical problems
		8.7 Solve numerical problems
<b>14</b> <sup>th</sup>		TUTORIAL CLASS
		FILTERS:
		9.1 Define filter
		<ul><li>9.2 Classification of pass Band, stop Band and cut-off frequency.</li><li>9.3 Classification of filters.</li></ul>
		9.4 Constant – K low pass filter
		9.5 Constant – K high pass filter.
		9.6 Constant – K Band pass filter.
		9.7 Constant – K Band elimination filter.
15 <sup>th</sup>		
		9.8 Solve Numerical problems
•	-	·

	TUTORIAL CLASS